

Unit - 2Feedback

It is the process of feeding back some part of the output signal into the input of the circuit through a suitable network.

Types of Feedback

(i) Positive feedback →

The feedback signal has the same phase as of V_{in} signal.
Also called as regenerative / direct feedback.

(ii) Negative feedback →

The feedback signal has the opposite phase of V_{in} signal.
Also called as degenerative / inverse feedback.

Ans Negative feedback derivation (gain with/without feedback)

(open loop)


$$A_o = \frac{V_o}{V_i}$$

(closed loop gain)

$$A_f = \frac{V_o}{V_s}$$

$$V_i = V_s - V_f$$

$$V_o = V_i + V_f$$

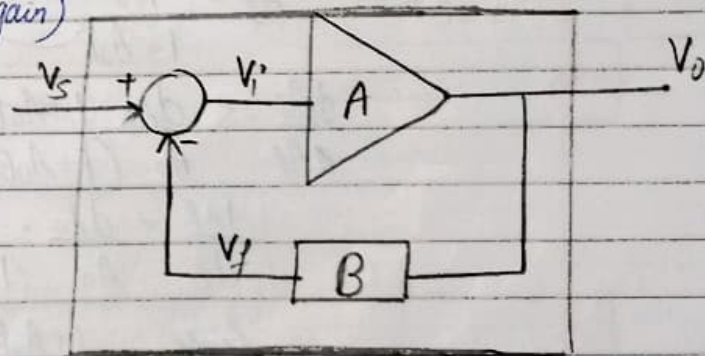

Feedback Amplifier

$$A_f = \frac{V_o}{V_s} \Rightarrow \frac{V_o}{V_i + V_f} \Rightarrow \frac{V_o}{V_i + B V_o}$$

divide numerator & denominator by V_i

$$A_f = \frac{V_o}{V_i} \div \frac{V_i + B V_o}{V_i}$$

$$A_f = A_o \div 1 + B A_o$$

$$\boxed{A_f = \frac{A_o}{1 + B A_o}}$$

Ques

Prove that the stability of the gain A_f of an amplifier with negative feedback increases by a factor $1+A_oB$ compared to that of an amplifier without feedback, where A_o is open loop & B is feedback factor.

$$A_f = \frac{A_o}{1+A_oB}$$

$$\frac{dA_f}{dA_o} = \frac{(1+A_oB) \frac{dA_o}{dA_o} - A_o \frac{d(1+A_oB)}{dA_o}}{(1+A_oB)^2}$$

$$\frac{dA_f}{dA_o} = \frac{(1+A_oB) - A_oB}{(1+A_oB)^2} \Rightarrow \frac{1}{(1+A_oB)^2}$$

$$dA_f = \frac{dA_o}{(1+A_oB)^2}$$

divide both sides by A_f .

$$\frac{dA_f}{A_f} = \frac{dA_o}{A_o (1+A_oB)^2}$$

w.k.t, $A_f = \frac{A_o}{1+A_oB}$

$$\frac{dA_f}{A_f} = \frac{dA_o}{A_o} \cdot \frac{1}{(1+A_oB)^2}$$

$$\boxed{\frac{dA_f}{A_f} = \frac{dA_o}{A_o} \cdot \frac{1}{(1+A_oB)^2}}$$

Since, $1+A_oB \gg 1$, $\Rightarrow 1+A_oB \approx A_oB$

$$\boxed{\frac{dA_f}{A_f} = \frac{dA_o}{A_o} \cdot \frac{1}{A_oB}}$$

$\frac{dA_f}{A_f} \rightarrow$ fractional change in amplification with feedback

$\frac{dA_o}{A_o} \rightarrow$ fractional change in amplification without feedback

RC Phase shift oscillator

It consists of a common emitter single-stage amplifier with a phase shift feedback network consisting of 3 identical RC sections.

It is suitable for low frequency applications.

Principle of working of RC phase shift oscillator

- (i) The total phase shift around the loop must be 360° .
- (ii) Along with the 180° phase shift with the ~~oscill~~ amplifier, the oscillator gives a 180° phase shift, & so, the total phase shift is $360^\circ \approx 0^\circ$.


Barkhausen condition for oscillations (Gain Equation)


- (i) Loop gain = one in absolute magnitude, i.e., $|BA| = 1$
- (ii) The phase shift is either zero / multiple integral multiple of $2\pi n$, $n = 0, 1, 2, \dots$

$$f = \frac{1}{2\pi RC\sqrt{6}} \quad \left[\frac{R}{29} \right]$$

$$A_v \geq 29$$

Working of RC Phase shift oscillator

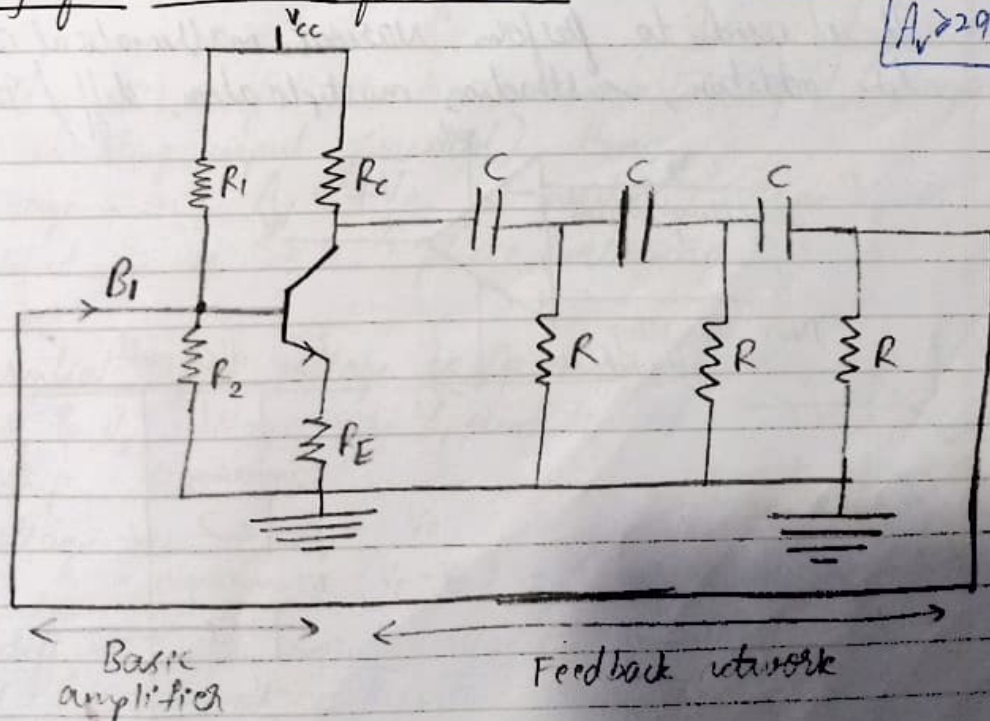


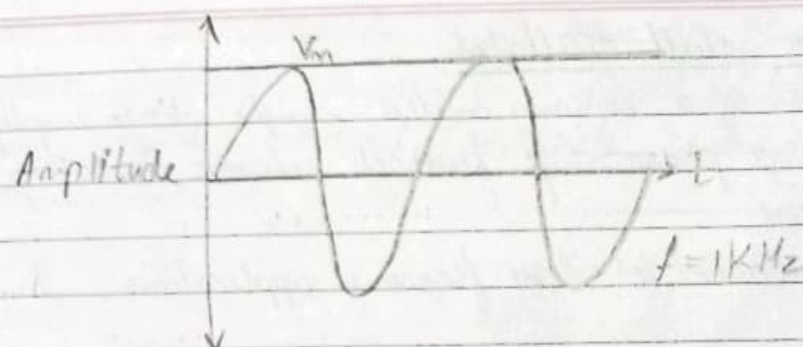

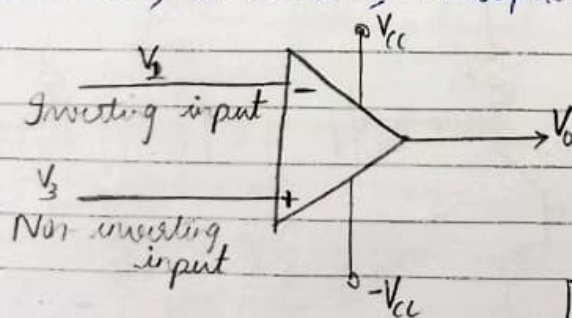- (i) RC oscillator consists of amplifier & feedback network.
- (ii) The capacitors & Resistors are arranged in a ladder fashion.
- (iii) A single RC section can provide a max phase shift of 90° . So, a minimum of 2 RC sections is required for 180° phase shift.
- (iv) In practical, each RC section provides a phase shift of 60° . So, for 180° phase shift, we will need 3 RC sections.


Operational Amplifier

- It is a direct coupled, multistage, voltage amplifier with extremely high gain.
- It is available in IC form.
- It is used to perform various mathematical calculations like addition, subtraction, multiplication, diff/Integration.




	offset null	No connection
1		8
Inverting (-)		
2		7
Noninverting (+)		
3		6
-Vcc		
4		5
		offset null

Op-amp in inverting mode (-)

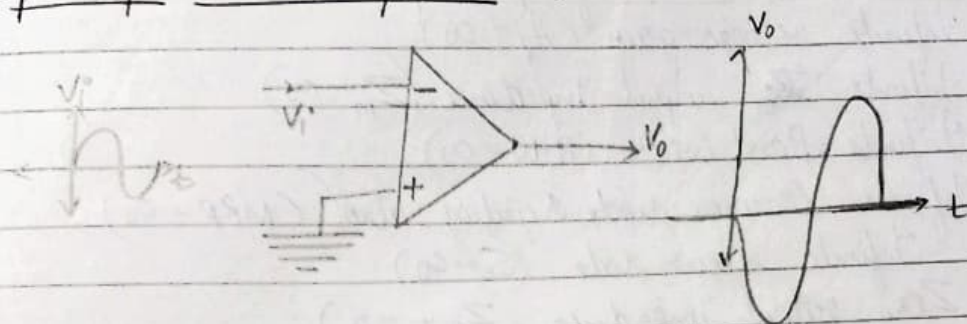

- If a voltage (V_i) is applied at the inverting input, keep non-inverting input as grounded, then
- Voltage gain $A_v = \frac{-V_o}{V_i}$ is negative, where (V_o) is inverted by 180° & V_i amplitude amplified.


Op-amp as non-inverting mode (+)

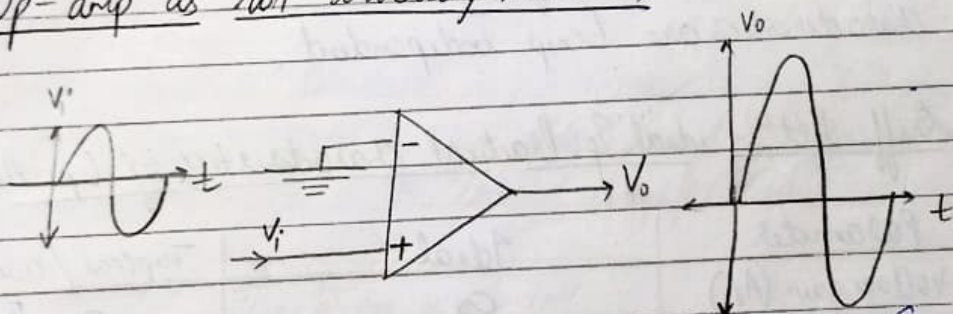

- If voltage (V_i) is fed at the non-inverting input, (keeping the inverting input grounded), then,
- Voltage gain, $A_v = \frac{+V_o}{V_i}$ is positive, where V_o is amplified & is in V_i phase with input.

Differential input voltage to Op-amp

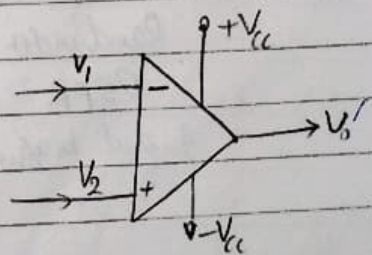- When V_1 & V_2 voltages are applied to the Op-Amp, then
- voltage gain $\Rightarrow A_v = \frac{V_o}{(V_1 - V_2)}$



- The diff bet^w the input voltages is amplified. So, Op-Amp is called "High gain differential amplifier".


Ideal characteristics of Op-Amp

- 1) Infinite voltage gain ($A_v = \infty$)
- 2) Infinite Z_{in} input impedance ($Z_{in} = \infty$)
- 3) Infinite Band width ($B.W = \infty$)
- 4) Infinite common mode rejection ratio ($CMRR = \infty$)
- 5) Infinite slew rate ($S = \infty$)
- 6) Zero output impedance ($Z_{out} = 0$)
- 7) Zero power supply rejection ratio ($PSRR = 0$) [Output voltage is zero when power supply = 0]
- 8) Zero offset voltage [if input voltage = zero, output voltage = 0]
- 9) Perfect Balance [$V_o = 0$, if the input voltages at the two terminals are equal]
- 10) Characteristics are temp independent.

Diff bet^w ideal & practical characteristics of Op-Amp

Parameter	Ideal	Typical / Practical value
Voltage gain (A_v)	∞	2×10^5
Z_{out}	0	75 Ω
Z_{in}	∞	2M Ω
Input offset	0	2mV
CMRR	∞	90dB
Slew rate	∞	0.5V μs^{-1}
Bandwidth	∞	1MHz
PSRR	0	30 $\mu V/V$
Input bias current	0	80 nA

Weg Wein - Bridge Oscillator

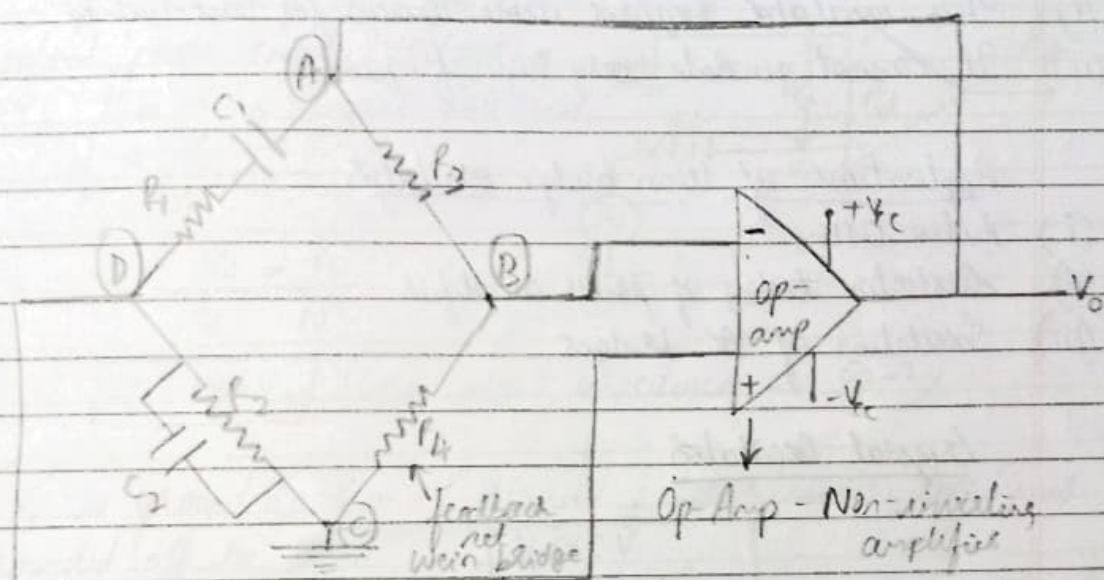

- Weg Wein Bridge Oscillator is an electronic device that generates sine waves.
- Wein Bridge Oscillator = Wein bridge circuit + differential amplifier
- It is a two staged RC coupled amplifier circuit.

Working of Wein bridge oscillator

- (i) It is made up of 4 resistors & 2 capacitors. The component values of both RC circuits are same.
- (ii) At lower frequencies, reactance of capacitors is very high. C_1 acts as open circuit & output voltage is 0.
- (iii) At high frequencies, reactance of capacitors is very low. R_2 is short circuited & output voltage is 0.
- (iv) At resonant frequency, phase shift betw input & output will be zero. Max output voltage is observed. $V_0 = V_i/3$

Adv of Wein bridge oscillator

- (i) Overall gain of oscillator is high as it uses two-stage amplifier
- (ii) Wein bridge oscillator has good frequency stability


Disadvantages of Wein bridge oscillator

- (i) This oscillator requires more devices for construction.
- (ii) It cannot generate very high frequencies.

Applications of Wein bridge oscillator

- (i) Audio testing
- (ii) Distortion testing of power amplifiers
- (iii) Excitation of AC bridges.

Crystal Oscillator

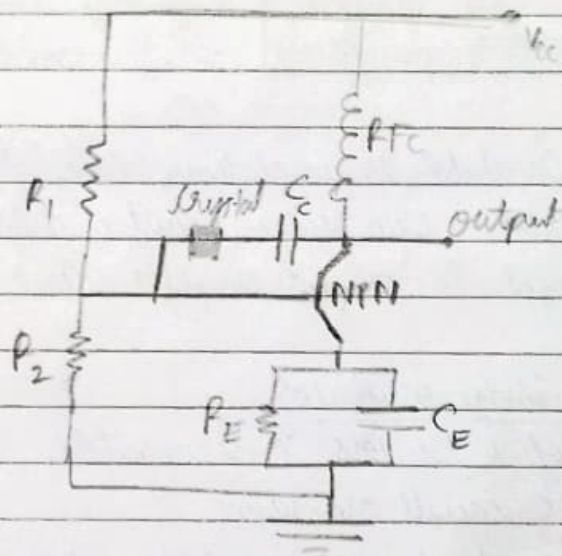

- (i) It is a device that uses the inverse piezoelectric effect to convert vibrations into stable oscillations.
- (ii) It applies an alternating voltage to a crystal, which makes the crystal vibrate at natural frequency.
- (iii) The oscillator can be designed to operate in low-impedance mode/high-impedance mode.
- (iv) The oscillator offers excellent frequency stability.
- (v) These oscillators are used in devices like GPS, microprocessors.

Concept of Virtual Ground


(i) Op-Amp has very high gain. (Order $= 10^5$)

(ii) If output power supply voltage is $+15V$, then max input voltages,

$$A_d = \frac{V_o}{V_i}$$

$$V_i = \frac{V_o}{A_d} = \frac{15}{10^5}$$

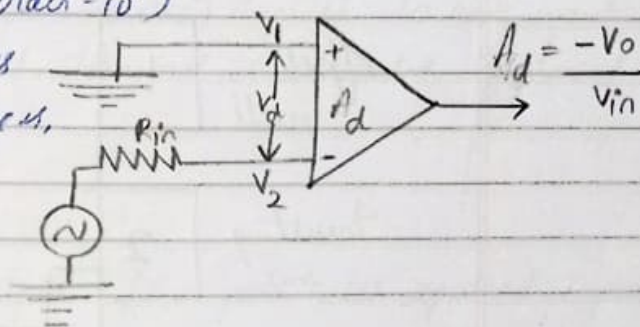
$$\boxed{V_i = 150 \mu V} \quad (\text{When input impedance is } \infty)$$



(iii) If V_1 is grounded, then $V_2 \neq 150 \mu V$. This is very less & is rounded off to zero. $\therefore V_2 \approx 0V$

(iv) But it is not really grounded & so it is called virtually grounded.


Voltage Transfer Characteristics

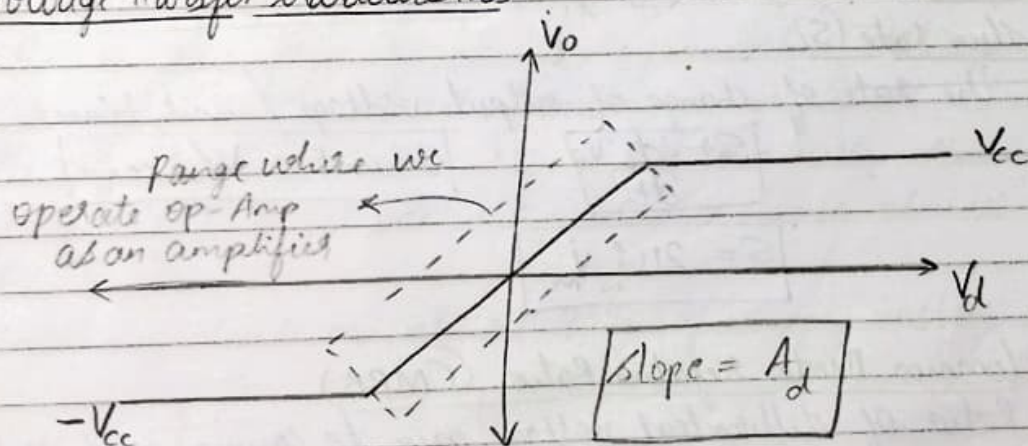

Applications of Op-Amp

- (i) Amplifier
- (ii) Adders & subtractors
- (iii) Integrators & differentiators
- (iv) Clock generators
- (v) Oscillators
- (vi) Inverting & Non-inverting Amplifiers

Pin diagram of 741 Op-Amp

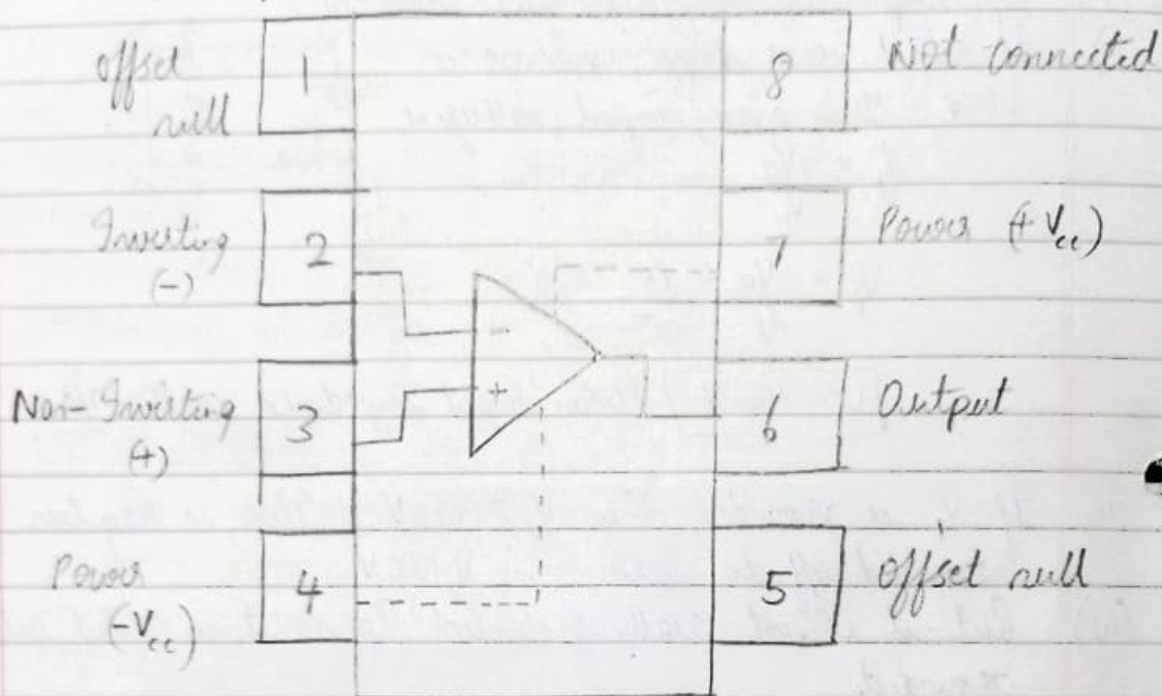

Terms

(i) Slur rate (S)

The rate of change of output voltage / unit time

$$S = \frac{dV_o}{dt}$$

$$S, \text{ unit} = V/\mu\text{sec}$$

$$S = 2\pi f_m V_m$$

(ii) Common Mode Rejection Ratio (CMRR)

Ratio of differential voltage gain to common mode voltage gain

$$CMRR = \frac{A_d}{A_c}$$

$$CMRR = 20 \log \left(\frac{A_d}{A_c} \right) \text{ dB}$$

$$CMRR = A_d - A_c$$

(iii) Open loop voltage gain (A_o)

Ratio of output voltage to input voltage in the absence of feedback.

$$A_v = \frac{V_o}{V_i}$$

$$A_v = 2 \times 10^5$$

(iv) Input Impedance (Z_i)

The impedance seen by the input (source) Applied to one input terminal when the other input terminal is connected to ground.

$$Z_i \approx 2M\Omega$$

(v) Output Impedance (Z_o)

The impedance given by the output for a particular applied input

$$Z_o = 75\Omega$$


(vi) Power Supply Rejection Ratio (PSRR)

Defined as the change in the output voltage / unit changes in DC supply voltage

$$PSRR = \frac{\Delta V_o}{\Delta V_{cc}}$$


Saturable property of Op-Amp

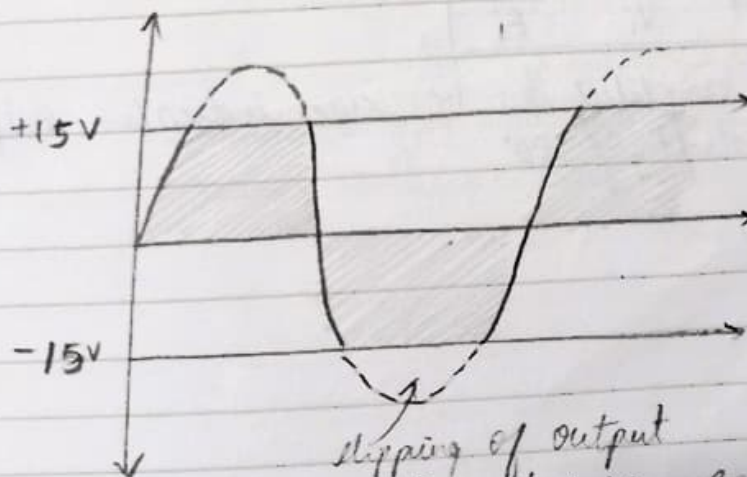- It is the prop of an Op-Amp in which voltage is swinging betⁿ saturation voltages $+V_{cc}$ & $-V_{cc}$
- If V_o rises more than $+V_{cc}$ / less than $-V_{cc}$ then it gets clipped off & gets saturated at the levels almost equal to $+V_{cc}$ & $-V_{cc}$
- Saturation levels are almost 90% of supply voltage levels.



clipping of output
due to saturable property

1) Inverting Amplifier

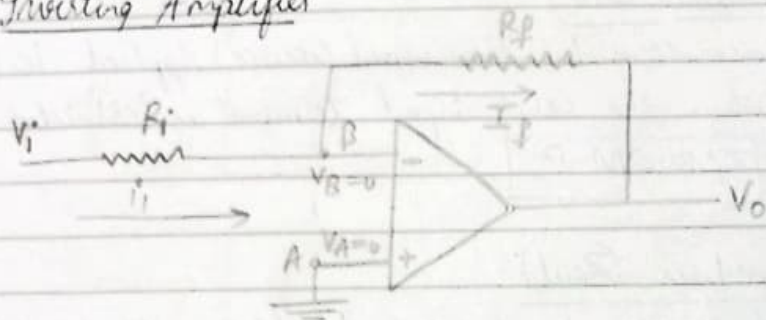

- (i) Non-inverting terminal is grounded & input signal is applied at inverting terminal.
- (ii) By virtual grounding, $V_B = V_A = 0 \text{ V}$
- (iii) Due to high Z_{in} of op-amp, current flowing through inverting terminal is zero.
- (iv) At point B,

$$I_i = I_f$$

$$\frac{\Delta V}{R} = \frac{\Delta V}{R}$$


$$\frac{V_i - V_B}{R_i} = \frac{V_B - V_o}{R_f} \Rightarrow \frac{V_i}{R_i} = \frac{0 - V_o}{R_f}$$

$$\frac{V_i}{R_i} = -\frac{V_o}{R_f}$$

Rearranging the terms, we get

$$A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

$\frac{R_f}{R_i}$ is gain of amplifier & $(-ve)$ sign indicates output is under phase shift of 180°

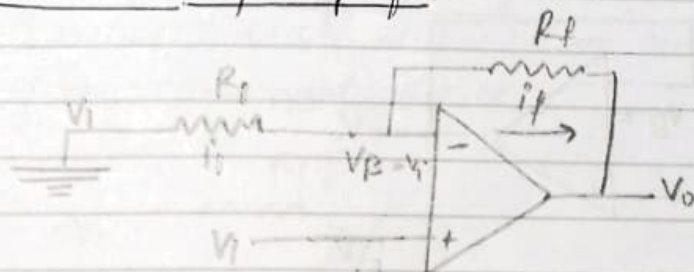2) Non-Inverting Amplifier

- (i) Input signal is applied to non inverting terminal & inverting terminal is grounded through R_i
- (ii) Due to virtual grounding,
 $V_i = 0 \rightarrow V_B = 0$ & $V_B = V_i$ & $V_i = 0$
- (iii) Due to high input impedance of Op-Amp,

$$i_i = i_f$$

$$\frac{\Delta V}{R} = \frac{\Delta V}{R} \Rightarrow \frac{V_i - V_B}{R_i} = \frac{V_B - V_o}{R_f}$$

$$\Rightarrow \frac{0 - V_B}{R_i} = \frac{V_B - V_o}{R_f} \Rightarrow \frac{-V_i}{R_i} = \frac{V_i - V_o}{R_f}$$

$$\Rightarrow \frac{-V_i}{R_i} = \frac{V_i}{R_f} - \frac{V_o}{R_f}$$

$$\Rightarrow \frac{V_o}{R_f} = \frac{V_i}{R_f} + \frac{V_i}{R_i}$$


$$\frac{V_o}{R_f} = V_i \left[\frac{1}{R_i} + \frac{1}{R_f} \right]$$

$$\frac{V_o}{V_i} = R_f \left[\frac{1}{R_i} + \frac{1}{R_f} \right]$$

$$A_v = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$

$$\beta = \frac{R_i}{R_i + R_f}$$

3) Voltage follower

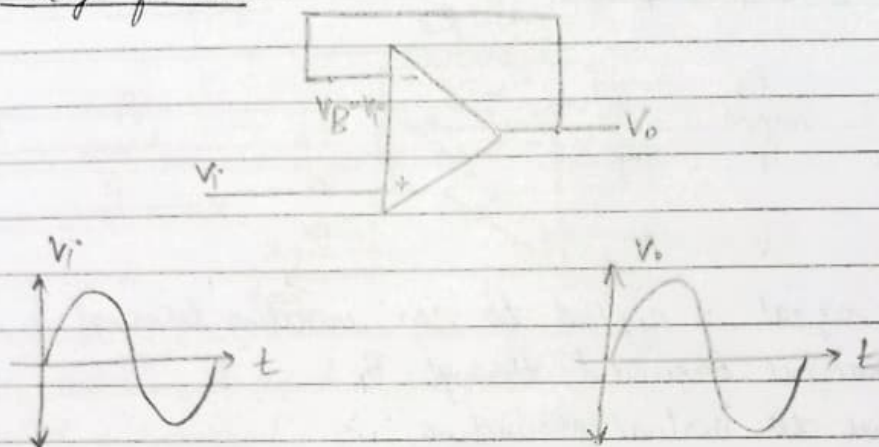

- It is obtained by short circuiting R_f & open circuiting R_i
- All the output is feedback to the inverting terminal
- When $R_f = 0$ & $R_i = \infty$,
 $V_o = V_i$ (Virtual ground)
- Inverting terminal is directly connected to output
 $V_o = V_i$

$$\therefore \boxed{V_i = V_o}$$

$$\text{Also, } \boxed{A_v = \frac{V_o}{V_i} = 1}$$

Feedback of voltage follower,

$$A_f = \frac{A_o}{1 + \beta A_o}, \quad \boxed{\beta = 1}$$


$$\boxed{A_f = \frac{A_o}{1 + A_o}} \text{ gain of voltage follower}$$

$$\text{Error} = \left[\frac{1 - A_o}{1 + A_o} \right] \times 100 = \%$$

- The voltage follower is non-inverting amplifier with voltage gain of unity

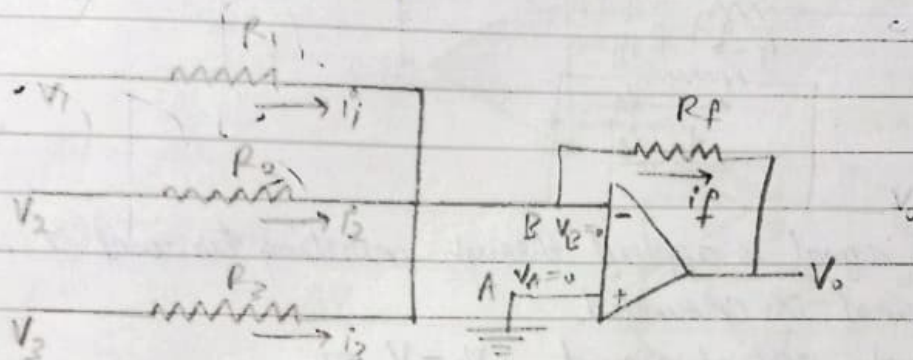4) Summing Inverting Op-Amp

Inverting ladder is one whose output is the inverted sum of the constituent inputs.



$$i_1 = \frac{\Delta V}{R_1} = \frac{V_1 - V_B}{R_1} \Rightarrow \frac{V_1 - 0}{R_1} = \frac{V_1}{R_1}$$

$$i_2 = \frac{\Delta V}{R_2} \Rightarrow \frac{V_2 - V_B}{R_2} \Rightarrow \frac{V_2 - 0}{R_2} = \frac{V_2}{R_2}$$

$$i_3 = \frac{\Delta V}{R_3} \Rightarrow \frac{V_3 - V_B}{R_3} \Rightarrow \frac{V_3 - 0}{R_3} = \frac{V_3}{R_3}$$

$$i_f = \frac{\Delta V}{R_f} \Rightarrow \frac{V_B - V_0}{R_f} \Rightarrow \frac{0 - V_0}{R_f} = \frac{-V_0}{R_f}$$

Apply KCL at point B,

$$i_f = i_1 + i_2 + i_3$$

$$\frac{-V_0}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$


$$V_0 = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

Scalar Scaling
Eqn

If $R_1 = R_2 = R_3 = R_f$

$$V_0 = - [V_1 + V_2 + V_3]$$

Average (V₀) Eqn

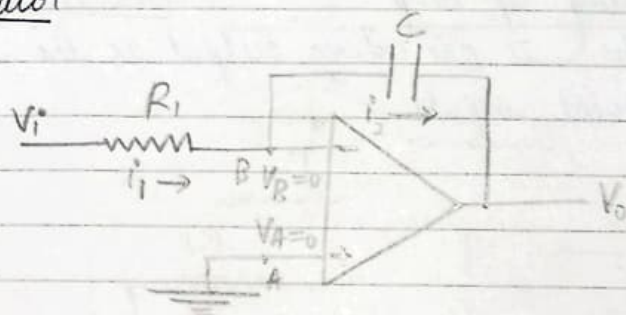5) Integrator

- Input signal is applied through inverting terminal & non-inverting terminal is grounded.
- Through virtual ground $V_B = V_A = 0$
- Apply Kcl at point B,

$$i_1 = i_2$$

$$\frac{\Delta V}{R} = C \frac{dV}{dt}$$

$$\frac{V_i - V_B}{R_1} = C \cdot \frac{dV_o}{dt}$$

$$\frac{V_i}{R_1} = C \frac{dV_o}{dt} (V_B - V_o)$$

$$\frac{V_i}{R_1} = -C \frac{dV_o}{dt}$$

$$\int \frac{dV_o}{dt} = \int \frac{-V_i}{R_1 C} dt$$

$$V_o = \frac{-1}{R_1 C} \int_0^t V_i dt + V_o(0)$$


$$V_o = \frac{-1}{R_1 C} \int_0^t V_i dt$$

output voltage for integrator

- $V_o(0)$ is the initial voltage on capacitor at $t=0$, (its const)
- There a phase shift of 180° bet^{wn} input & output signals

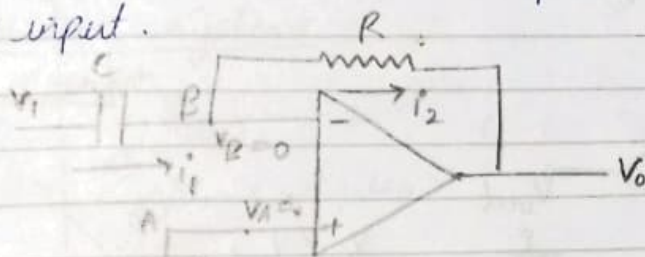6) Differentiator

A differentiator is one whose output is the differentiation of the input.



→ Input signal is applied through inverting terminal & non-inverting terminal is grounded

→ Through virtual grounding,

$$V_A = V_B = 0$$

→ Apply KCL at point B,

$$I_1 = I_2$$

$$\frac{C \cdot dV}{dt} = \frac{V}{R}$$

$$C \cdot \frac{d(V_1 - V_B)}{dt} = \frac{V_B - V_0}{R}$$


$$C \cdot \frac{dV_1}{dt} = \frac{-V_0}{R} \quad (V_B = 0)$$

$$V_0 = -RC \cdot \frac{dV_1}{dt}$$

→ Output is $(-RC)$ times the differential of input. We observe a phase shift of 180° bet^{wn} input & output signal.

→ Main adv of differentiator is the small time constant required for differentiation

Comparator

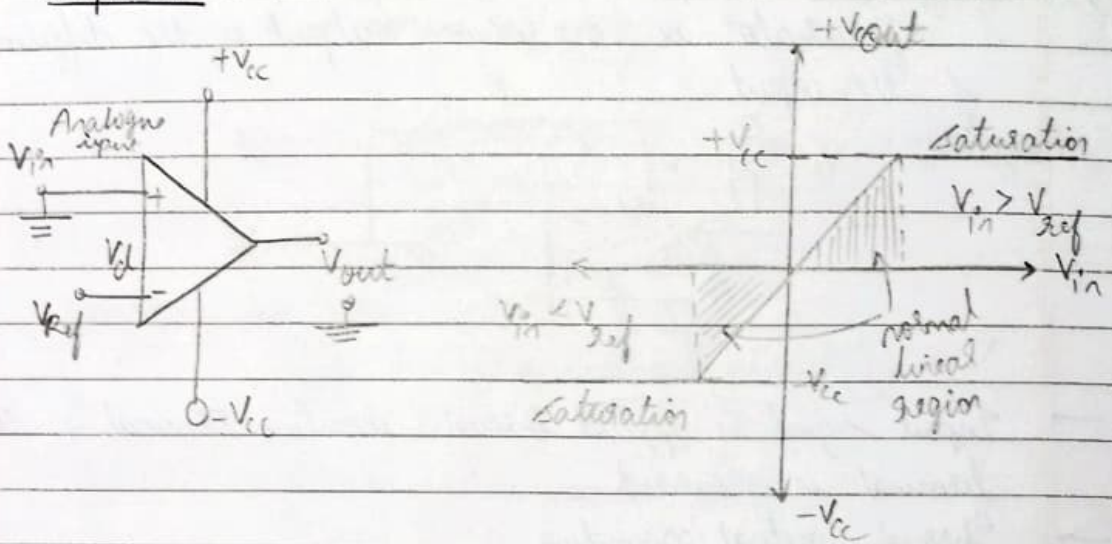

Graph of Comparator

