
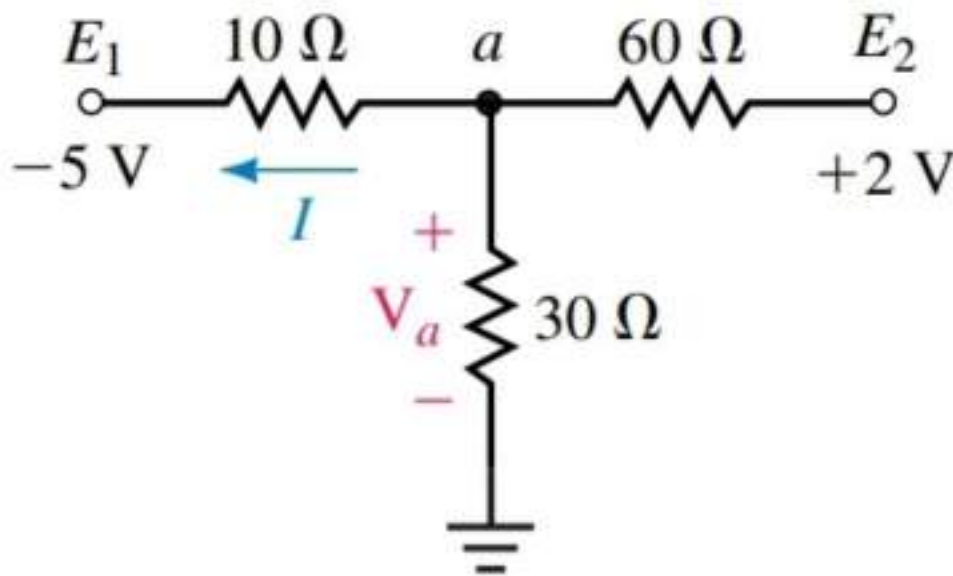


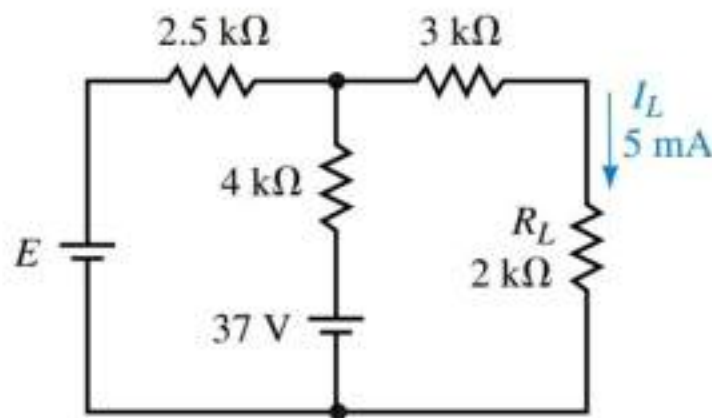(1Q) Find the voltage V_a and current I in the following circuit.



(2Q)


Given the circuit of Figure 9-79, what must be the value of the unknown voltage source to ensure that the current through the load is $I_L = 5 \text{ mA}$ as shown. Verify the results using superposition.




“

Please ignore the last sentence (superposition)!”

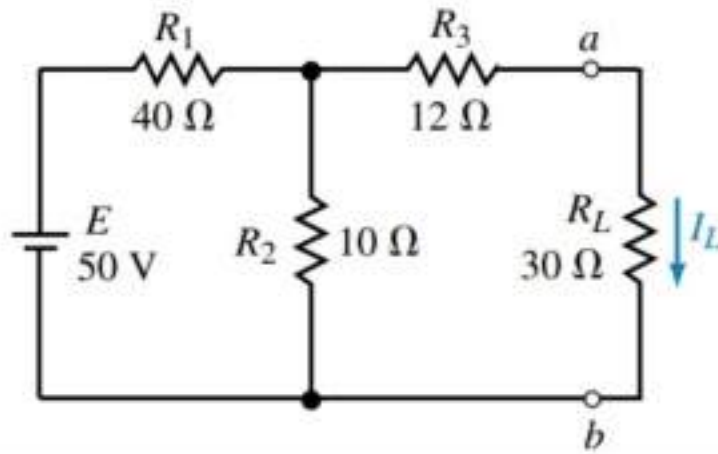
Find the Thévenin equivalent external to R_L in circuit of Figure 9–81. Use the equivalent circuit to find V_{ab} .



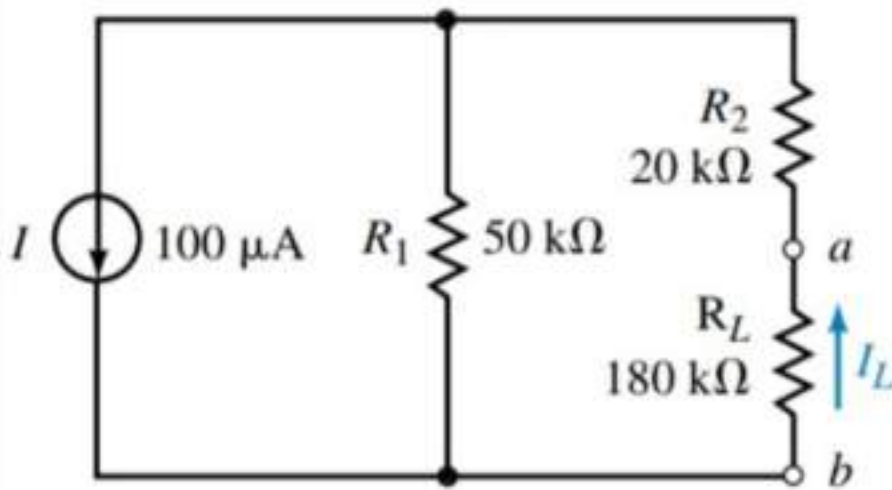(Q) Find the thevenin equivalent circuit for the following networks.




(a)

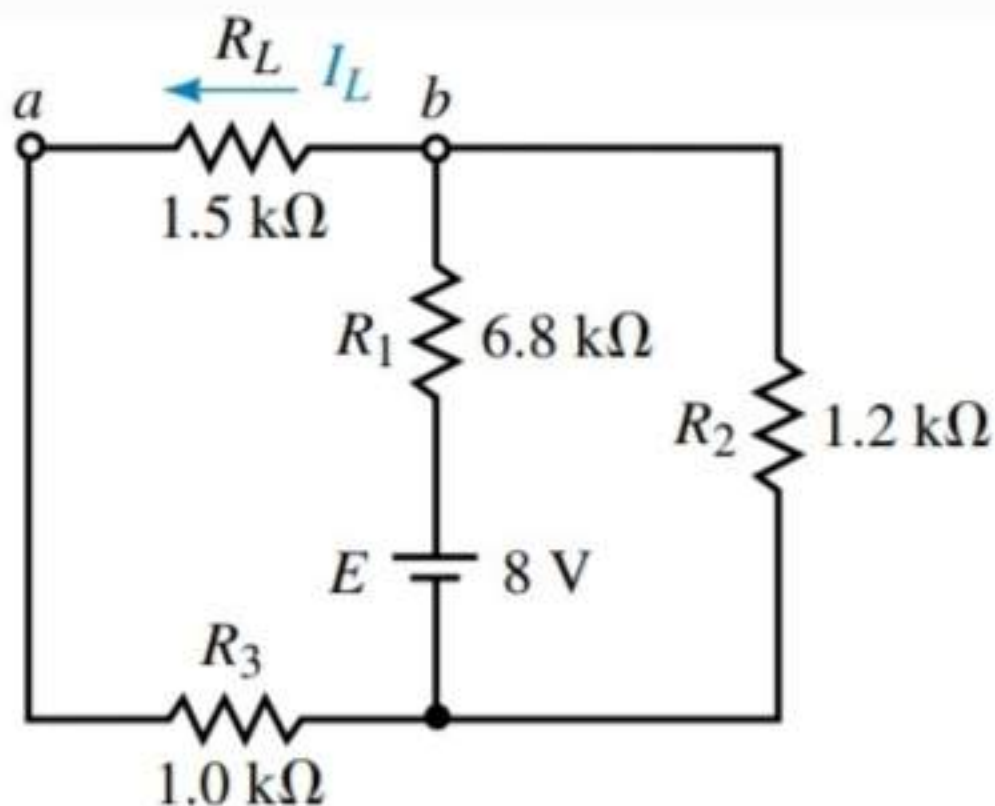

(b)

Refer to the circuit of Figure 9–87:

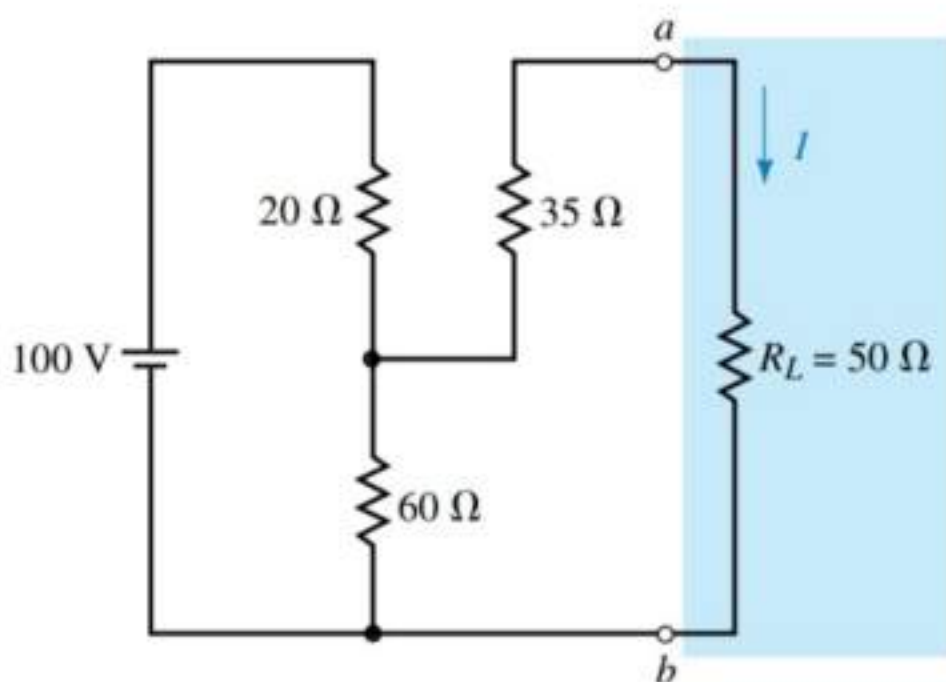- Find the Thévenin equivalent circuit external to the indicated terminals.
- Use the Thévenin equivalent circuit to determine the current through the indicated branch.



Refer to the circuit of Figure 9–89:

- Find the Thévenin equivalent circuit external to the indicated terminals.
- Use the Thévenin equivalent circuit to determine the current through the indicated branch.

