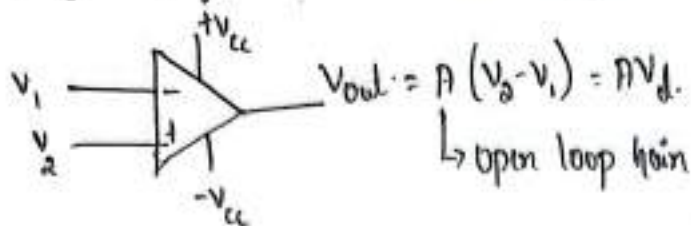


Op-amp:


①

Large no of amplifiers are cascaded together \rightarrow gain is infinite.




When 1p is applied to inverting terminal with non-inverting terminal being grounded then

$$V_{out} = A(0 - v_1) = -Av_1$$

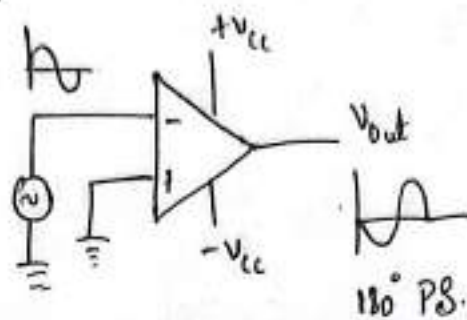

When 1p is applied to non inverting terminal with inverting terminal being grounded then

$$V_{out} = Av_2$$

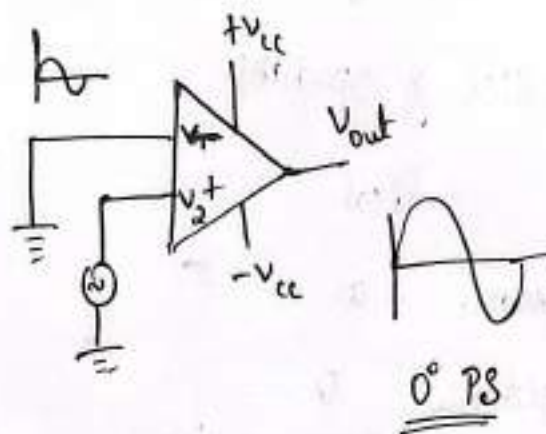

Common mode 1p vtg $V_{icm} = \frac{v_1 + v_2}{2}$

Differential 1p vtg $V_{id} = v_2 - v_1$

$$\text{Thus } v_1 = V_{icm} - \frac{V_{id}}{2}$$

$$v_2 = V_{icm} + \frac{V_{id}}{2}$$

$$\therefore V_o = A_d V_{id} + A_{cm} V_{icm}$$

Problems:

i) $V_2 = 0V$, $V_0 = 2V$, $A = 10^3$, $V_1 = ?$, $V_{icm} = ?$, $V_{id} = ?$

$$V_0 = A(V_2 - V_1) \Rightarrow V_2 - V_1 = \frac{V_0}{A} \Rightarrow V_1 = V_2 - \frac{V_0}{A} = 0 - \frac{2}{10^3} = \underline{\underline{-2mV}}$$

$$V_{icm} = \frac{V_1 + V_2}{2} = \underline{\underline{-1mV}}$$

$$V_{id} = V_2 - V_1 = \underline{\underline{2mV}}$$

ii) $A = 10^3$, $V_2 = 5V$, $V_0 = -10V$, $V_1 = ?$, $V_{icm} = ?$, $V_{id} = ?$

$$\text{Sol}^n: V_1 = V_2 - \frac{V_0}{A} = 5 + \frac{10}{10^3} = 5 + \frac{1}{100} = 5 + 0.01 = \underline{\underline{5.01V}}$$

$$V_{icm} = \frac{V_1 + V_2}{2} = \underline{\underline{5.005V}}$$

$$V_{id} = V_2 - V_1 = 5 - 5.01 = \underline{\underline{-0.01V}} = \underline{\underline{-10mV}}$$

Characteristics of OP-Amp

Ideal

Practical

i) ip impedance ∞

$2M\Omega$

ii) Op impedance 0

$50-100\Omega$

iii) V_{tg} gain ∞

2×10^5

iv) Bandwidth ∞

$1MHz$

[gain should be constant over the entire range]

v) CMRR ∞

$86dB-100dB$

$$CMRR = \frac{A_d}{A_{cm}}$$

Common mode sigs

Should be rejected thus $A_{cm} = 0$

$$\therefore CMRR = \frac{A_d}{0} = \infty$$

(2)

vi) Slew Rate

 ∞ 1V/ μ s @ 10V/48.

It is a measure of how fast the op-amp's o/p can change in response to the changes in i/p level.

$$SR = \frac{dV_o}{dt}$$

SR limits the max operating frequency of the op-amp.

vii) i/p offset vlg.

0

2mV

viii) i/p offset current

0

20nA.

Let the O/p be a sinusoid $V_m \sin \omega t$.

$$\text{then } SR = \frac{dV_o}{dt} = V_m \omega \sin \omega t.$$

$$SR = V_m \omega$$

$$SR = V_m 2\pi f$$

$$f = \frac{SR}{2\pi V_m}$$

i) If $A=1$, $V_o = 10 \sin 3.14 \times 10^5 t$ calculate SR?

$$SR = \frac{dV_o}{dt} = 10(3.14 \times 10^5)$$

ii) $SR = 5V/\mu s$, $f = 200KHz$, $V_m = ?$

$$f = \frac{SR}{2\pi V_m} \Rightarrow V_m = \frac{SR}{2\pi f} = \frac{5}{2\pi (200K)} = 3.98V$$

iii) $SR = 3V/\mu s$, $V_m = 2$, calculate the max o/p freq so that o/p is not distorted.

$$f = \frac{SR}{2\pi V_m} = \frac{3}{2\pi \cdot 2} = 238KHz.$$


Virtual Short / Virtual Ground:

WKT $V_o = A(V_o - V_i)$ But $A = \infty$.

$$A = \frac{V_o}{V_o - V_i} = \infty \Rightarrow V_o - V_i = 0$$

$$\therefore V_o = V_i$$

i) Inverting Amplifier:

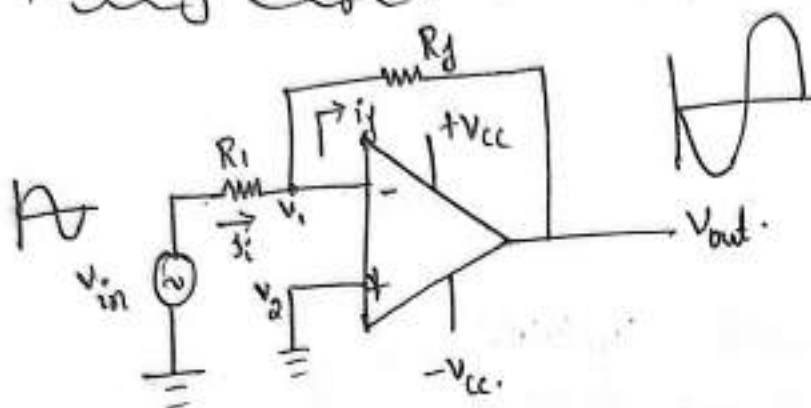

V_2 is grounded $\therefore V_2 = 0$.

Due to virtual short $V_1 = V_2$

Due to high \uparrow p impedance of op-amp current through op-amp is '0'.

Thus $I_i = I_f$.

$$\frac{V_1 - V_{in}}{R_i} = \frac{V_{out} - V_1}{R_f}$$


$$\frac{V_{in} - V_1}{R_i} = \frac{V_1 - V_{out}}{R_f}$$

But $V_1 = V_2 = 0$

$$\therefore \frac{V_{in}}{R_i} = -\frac{V_{out}}{R_f}$$

$$\boxed{\frac{V_{out}}{V_{in}} = A = -\frac{R_f}{R_i}}$$

Problems:

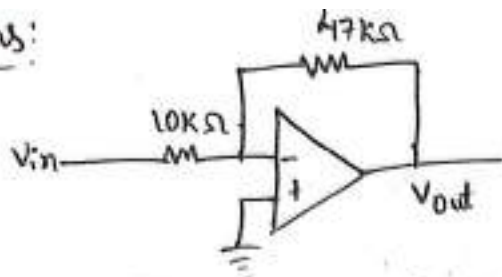

find A ?

$$A = -\frac{R_f}{R_i} = -\frac{47K}{10K} = -4.7 //$$

ii) A 200mV peak to peak sine wave is applied to an op-amp with $\frac{R_f}{R_i} = 10$. Sketch the o/p w/f.

$$\text{Sol: P-P} \rightarrow 2V_m = 200\text{mV}$$

$$V_m = 100\text{mV}$$

$$V_o = -\frac{R_f}{R_i} \times V_{in} = -1000\text{mV}$$


iii) Design an inverting amp with a closed loop v/g gain of -15

$$A_f = -15 = -\frac{R_f}{R_i}$$

$$R_f = 15R_i$$

$$\text{If } R_i = 1K\Omega \text{ then } R_f = \underline{15K\Omega}$$

Non-Inverting Amplifier:

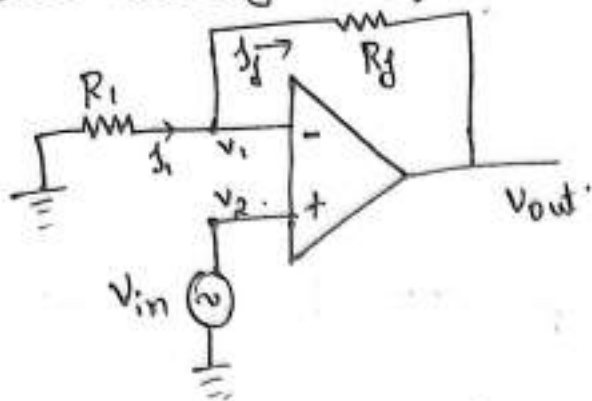

$$V_2 = V_1 = V_{in}$$

$$i_1 = i_f$$

$$\frac{V_1 - 0}{R_1} = \frac{V_{out} - V_1}{R_f}$$

$$\textcircled{a} \quad \frac{0 - V_1}{R_1} = \frac{V_1 - V_{out}}{R_f}$$

$$\text{But } V_1 = V_2 = V_{in}$$


$$\frac{-V_{in}}{R_1} = \frac{V_{in} - V_{out}}{R_f}$$

$$\frac{-V_{in}}{R_1} = \frac{V_{in}}{R_f} - \frac{V_{out}}{R_f}$$

$$\frac{V_{out}}{R_f} = \frac{V_{in}}{R_f} + \frac{V_{in}}{R_1} = V_{in} \left[\frac{1}{R_f} + \frac{1}{R_1} \right]$$

$$A = \frac{V_{out}}{V_{in}} = \underline{\underline{R_f \left[\frac{1}{R_f} + \frac{1}{R_1} \right]}} = \underline{\underline{1 + \frac{R_f}{R_1}}}$$

Voltage Follower:

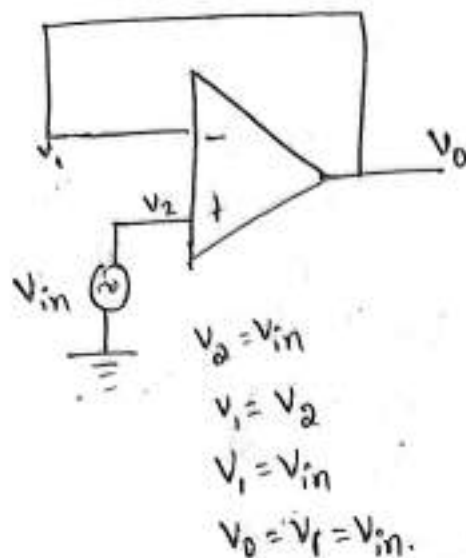

$$V_o = A V_d = A(V_2 - V_1) = A(V_{in} - V_o)$$

$$V_o = A V_{in} - A V_o$$

$$V_o(1+A) = A V_{in}$$


$$\frac{V_o}{V_{in}} = \frac{A}{1+A}$$

$$A = \frac{V_o}{V_{in}} = 1$$

→ O/P follows the I/P Vtg.

→ Derived from non-inverting amplifier by setting $R_1 = \infty$ & $R_f = 0$
 open Ckt. short Ckt.

Inverting Summing Ckt:

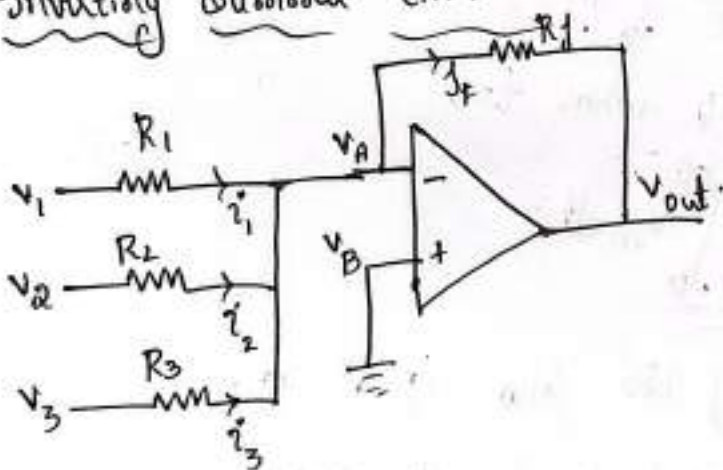


$$\text{But } V_A = V_B = 0$$

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_{out}}{R_f}$$

$$V_{out} = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

Integrator:

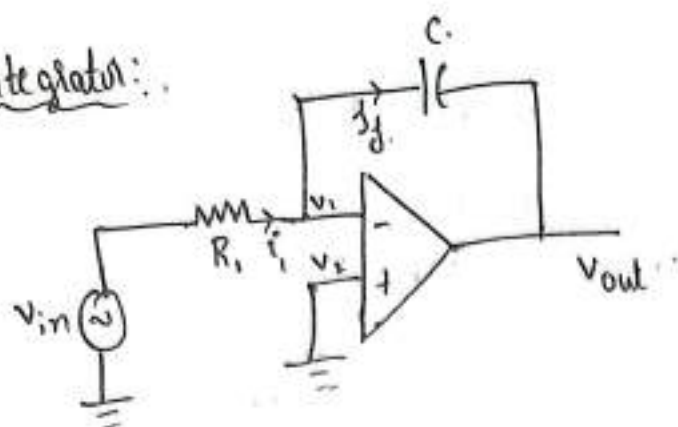

WKT $v_i = v_+ = 0$.

$$i_i = i_f$$

$$\frac{v_{in} - v_i}{R_i} = C \frac{d}{dt} (v_i - v_{out})$$

But $v_i = v_+ = 0$.

$$\therefore \frac{v_{in}}{R_i} = C \frac{d}{dt} (-v_{out})$$

$$\frac{v_{in}}{R_i} = -C \frac{dv_{out}}{dt}$$

$$\frac{dv_{out}}{dt} = -\frac{1}{R_i C} \left[\frac{v_{in}}{R_i} \right]$$

\int BS wkt t .

$$v_{out} = -\frac{1}{R_i C} \int_0^t v_{in} dt + v_o(0)$$


$v_o(0)$ is constant & $v_o(0) = 0$ when $t = 0$.

$$\therefore \underline{v_{out} = -\frac{1}{R_i C} \int_0^t v_{in} dt}$$

-ve sign indicates PS of 180° b/w i/p & o/p .

$R_i C$ is called time constant of the integrator.

Differentiator:

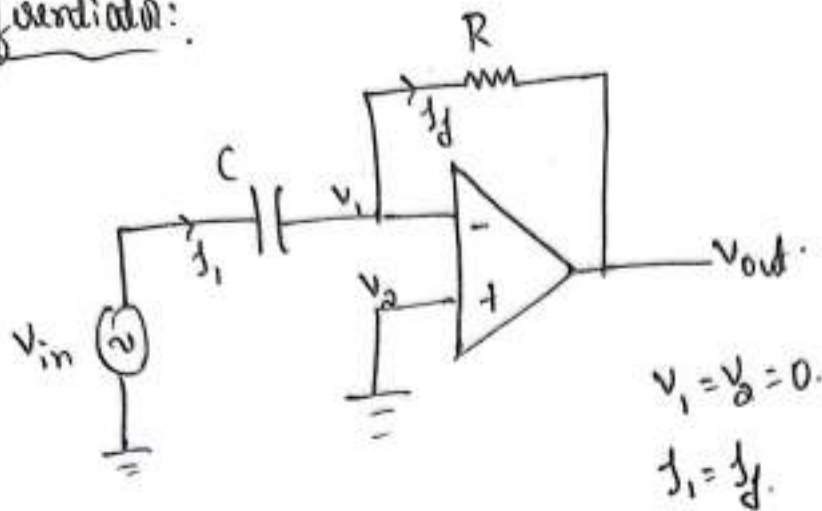

$$C \frac{d}{dt} (v_{in} - v_1) = \frac{v_1 - v_{out}}{R}$$

But $v_1 = v_2 = 0$

$$C \frac{d}{dt} (v_{in}) = -\frac{v_{out}}{R}$$

$$v_{out} = -R C \frac{d}{dt} (v_{in})$$

v_o is proportional to the derivative of v_{in} .

Design an adder circuit using an op-amp to obtain an o/p
 Expression $V_o = 2(0.1V_1 + 0.5V_2 + 20V_3)$ when V_1, V_2 & V_3 are i/p's.

Solⁿ: $V_o = 0.2V_1 + 1V_2 + 40V_3$.

Wkt $V_o = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3$.


Assuming $R_f = 10K\Omega$.

then $\frac{R_f}{R_1} = 0.2 \Rightarrow R_1 = \frac{10K\Omega}{0.2} = 50K\Omega$.

$\frac{R_f}{R_2} = 1 \Rightarrow R_2 = \frac{10K\Omega}{1} = 10K\Omega$.

$\frac{R_f}{R_3} = 40 \rightarrow R_3 = \frac{10K\Omega}{40} = 250\Omega$.

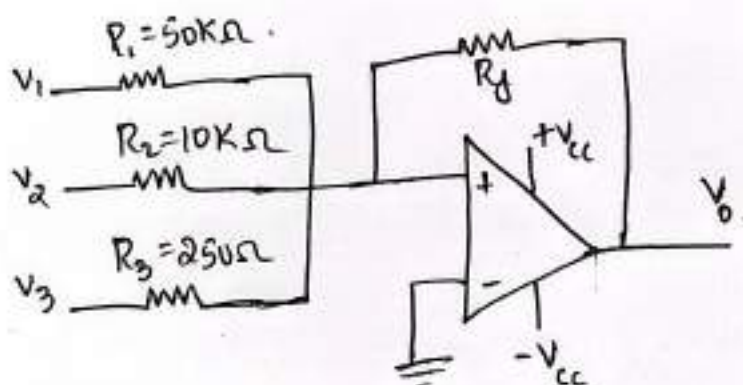The supply V_{cc} & -V_{cc} may be $\pm 15V$.



Design an adder circuit using op-amp to obtain an o/p vty
 given $V_o = -[0.5V_1 + 0.8V_2 + 2V_3]$.

Solⁿ: Wkt $V_o = -\left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right]$

$\frac{R_f}{R_1} = 0.5$ $\frac{R_f}{R_2} = 0.8$ $\frac{R_f}{R_3} = 2$.

Assume $R_f = 10K\Omega$.

$R_1 = \frac{10K}{0.5} = 20K\Omega$; $R_2 = \frac{10K}{0.8} = 12.5K\Omega$; $R_3 = \frac{10K}{2} = 5K\Omega$.

