

K-Maps [Karnaugh-Maps]

(3) 9

* Graphical method gives us a systematic approach for simplifying a Boolean expression.

* It contains boxes called cells.

Each of the cell represents one of the 2^n possible products that can be formed from 'n' variables.

2 Variable map $\Rightarrow 2^2 = 4$ cells.
(n=2)

3 Variable map $\Rightarrow 2^3 = 8$ cells.
(n=3)

4 Variable kmap $\Rightarrow 2^4 = 16$ cells.
(n=4)

2¹ 2⁰
0 0 \rightarrow 0
0 1
1 0
1 1
2¹ 2⁰

	B	\bar{B}	B
A	0	$\bar{A}\bar{B}_0$	$\bar{A}B_1$
\bar{A}	1	$A\bar{B}_2$	AB_3

2-Variable
k-map.

	BC	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
A	0	$\bar{A}\bar{B}\bar{C}_0$	$\bar{A}\bar{B}C_1$	$\bar{A}BC_3$	$\bar{A}B\bar{C}_2$
1	1	$A\bar{B}\bar{C}_4$	$A\bar{B}C_5$	ABC_7	$AB\bar{C}_6$

3-Variable
k-map.


	CD	00	01	11	10
AB	00	$\bar{A}\bar{B}\bar{C}\bar{D}_0$	$\bar{A}\bar{B}\bar{C}D_1$	$\bar{A}\bar{B}C\bar{D}_3$	$\bar{A}\bar{B}CD_2$
	01	$\bar{A}B\bar{C}\bar{D}_4$	$\bar{A}B\bar{C}D_5$	$\bar{A}BC\bar{D}_7$	$\bar{A}BCD_6$
	11	$AB\bar{C}\bar{D}_{12}$	$AB\bar{C}D_{13}$	$ABC\bar{D}_{15}$	$ABCD_{14}$
	10	$A\bar{B}\bar{C}\bar{D}_8$	$A\bar{B}\bar{C}D_9$	$A\bar{B}C\bar{D}_{11}$	$A\bar{B}CD_{10}$

\Rightarrow 4 Variable
k-map.

* Representation of Truth table on k-map.

EXOR :-


A	B	Y
0	0	0
0	1	1✓
1	0	1✓
1	1	0

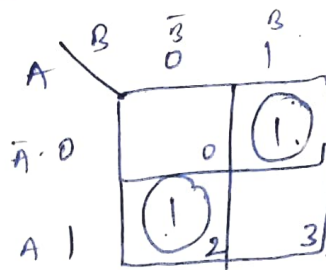

$$y = \bar{A}B + A\bar{B}$$


Full adder (Cont) :-

A	B	Cin	Cont
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1✓
1	0	0	0
1	0	1	1✓
1	1	0	1✓
1	1	1	1✓

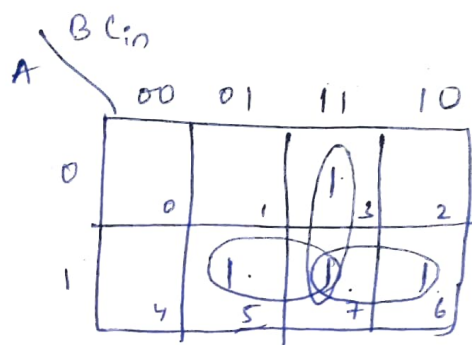

$$y = AB + BC_{in} + AC_{in}$$

Grouping in k-map :-

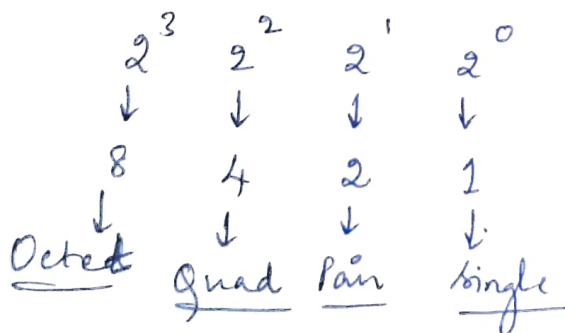

1) BC

A	00	01	11	10
0		1	1	
1				

\Rightarrow Grouping of 2 ones (Pair)

$$y = \bar{A}C$$

(2) BC

A	00	01	11	10
0			1	1
1	1			1

$$y = A\bar{C}$$

(3) BC

A	00	01	11	10
0		1	1	
1			1	

$$y = \bar{A}C + BC$$

(4) $y = \bar{A}\bar{B}C + \bar{A}BC + ABC + ABC\bar{C}$

BC

A	00	01	11	10
0		1	1	
1			1	1

(Pair not required)
(Redundant)

$$y = \bar{A}C + AB$$

(5) BC

A	00	01	11	10
0			1	1
1	1	1	1	1

$$y = A$$

(6) CD

AB	00	01	11	10
00			1	1
01		1	1	
11	1	1	1	1
10	1			1

$$y = BD$$

$$y = A\bar{D}$$

(7) Solve $y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD$

	CD	00	01	11	10
AB	00	1		3	2
	01		4	5	6
	11		12	13	14
	10	8	9	11	10

$y = \underline{\underline{\bar{B}\bar{D}}}$

~~(8) $y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{D} + \bar{A}\bar{C}$~~

(8) $y = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + \bar{A}B\bar{C}D + \bar{A}BCD + AB\bar{C}D + AB\bar{C}D + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD$

	CD	00	01	11	10
AB	00		1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$y = \underline{\underline{D}}$


(9) $y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D}$

	CD	00	01	11	10
AB	00	1	3	2	
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$y = \underline{\underline{\bar{B}}}$

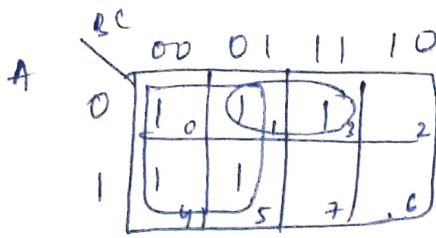
(10) Solve the Expⁿ using k-map.

$$y = A\bar{B}C + \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$$




$$y = \bar{A}C + \bar{B}$$

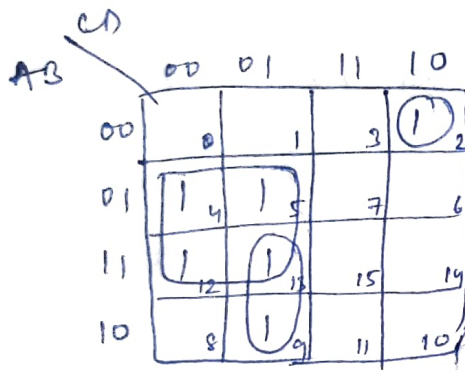(11) $y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D}$
 $+ \bar{A}\bar{B}C\bar{D}$




$$y = \bar{A}\bar{B}C\bar{D} + A\bar{C}D + B\bar{C}$$

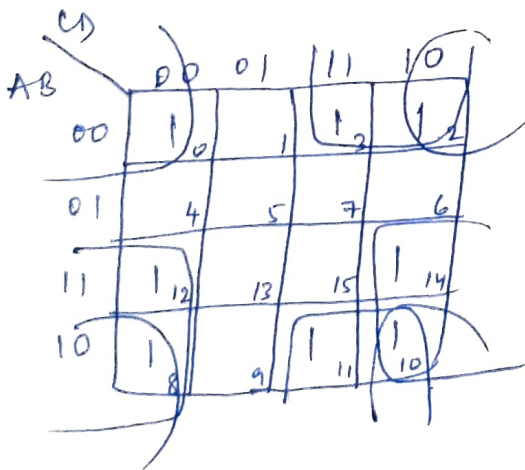(12) $y = \bar{A}\bar{B}C\bar{D} + ABC\bar{D} + A\bar{B}C\bar{D} + A\bar{B}CD + A\bar{B}\bar{C}\bar{D}$
 $+ AB\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}\bar{D}$, Realize using
 Logic circuit


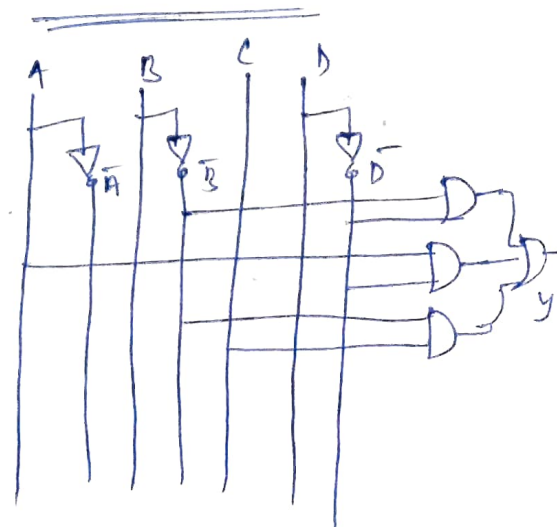
$$y = \bar{B}\bar{D} + A\bar{D} + \bar{B}C$$



$$(13) \quad Y = \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D + \bar{A}BCD + \bar{A}BC\bar{D} + \\ AB\bar{C}\bar{D} + AB\bar{C}D + ABCD + A\bar{B}CD$$

AB \ CD	00	01	11	10
00	0	1	3	2
01	4	1	1	1
11	1	1	1	1
10	8	9	1	10

$$Y = \bar{A}\bar{C}D + \bar{A}BC + AB\bar{C} + ACD$$

$$(14) \quad f(A, B, C, D) = \bar{A}\bar{B}D + AB\bar{C}\bar{D} + \bar{A}BD + AB\bar{C}\bar{D} \\ = \bar{A}\bar{B}D(C + \bar{C}) + AB\bar{C}\bar{D} + \bar{A}BD(C + \bar{C}) + AB\bar{C}\bar{D} \\ = \bar{A}\bar{B}DC + \bar{A}\bar{B}\bar{C}D + AB\bar{C}\bar{D} + \bar{A}BCD + \bar{A}B\bar{C}\bar{D} \\ + AB\bar{C}\bar{D}$$

AB \ CD	00	01	11	10
00	0	1	1	3
01	4	1	1	6
11	1	1	1	1
10	8	9	11	10

$$Y = \underline{\underline{AB\bar{D} + \bar{A}D}}$$


$$(15) \quad f(A, B, C, D) = \sum m(0, 1, 4, 8, 9, 10)$$

AB \ CD	00	01	11	10
00	1	1	3	2
01	1	5	7	6
11	1	1	1	1
10	1	1	1	1

$$f = \underline{\underline{\bar{A}\bar{C}\bar{D} + A\bar{B}\bar{D} + B\bar{C}}}$$


(19) $Y = \sum (0, 2, 6, 7, 8, 10, 14, 15)$

Ans : $\bar{B}\bar{D} + BC = Y$

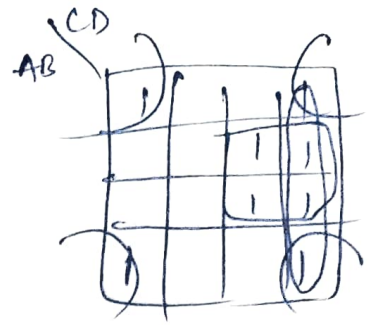

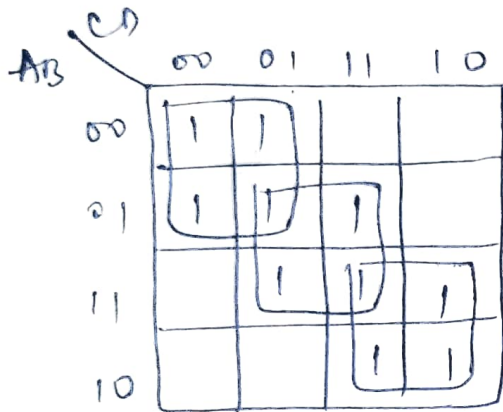
(20) Simplify the expⁿ using k-map and realize using Basic Gates

$Y = \sum m(0, 1, 4, 5, 7, 10, 11, 13, 14, 15)$



$Y = \bar{A}\bar{C} + BD + AC$

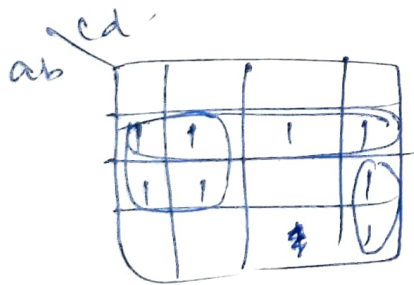(21) $Y(a, b, c, d) = \sum (4, 6, 12, 13, 14, 15, 7, 10)$



$Y = \bar{a}b + \bar{b}c + acd$

realize using gates

(22) $Y = ABCD + AB\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} + AB\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + ABC\bar{D} + A\bar{B}\bar{C}\bar{D}$

(23) $Y = \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}D + AB\bar{C}D + \bar{A}BCD + \bar{A}\bar{B}C\bar{D} + ABCD + A\bar{B}C\bar{D}$

(24) $f(x) = \sum (0, 2, 8, 10, 13, 15) + d_c(5, 7) \rightarrow \text{Ans : } BD + \bar{B}\bar{D}$