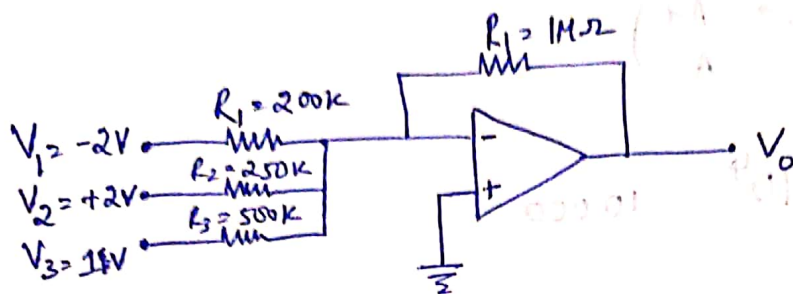


1) Calculate the output voltage of a three input summing Amplifier given:

$$R_1 = 200K\Omega, R_2 = 250K\Omega, R_3 = 500K\Omega, R_f = 1M\Omega, V_1 = -2V$$

$$V_2 = -2V, V_2 = +2V, V_3 = +1V.$$



Soln

For Summing Amplifier,

$$V_0 = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

$$= - \left[\frac{1 \times 10^6}{200 \times 10^3} (-2) + \frac{1 \times 10^6}{250 \times 10^3} (2) + \frac{1 \times 10^6}{500 \times 10^3} (1V) \right]$$

$$= - [-10 + 8 + 2]$$

$$= 0V$$

2) Op-amp has $A_d = 500$, CMRR of 80 dB, if common mode input is $2 \sin 10 \text{ at}$, calculate common mode output voltage.

Soln

$$CMRR = 20 \log \frac{A_d}{A_c}$$

$$80 = 20 \log \frac{A_d}{A_c}$$

$$4 = \log \left(\frac{A_d}{A_c} \right)$$

$$\frac{A_d}{A_c} = 10^4 = 10,000$$

~~$$A_c = \frac{10,000}{100,000} = 0.1$$~~

$$A_c = \frac{500}{10000} = 0.05$$

Common mode output voltage, $V_o = A_c \cdot V_c$

$$= 0.05 [2 \sin 100\pi t]$$

$$= 0.1 \sin 100\pi t$$

Q: open loop gain of op-amp is 10^4 and $A_c = 0.1$
calculate CMRR.

Soln

$$CMRR = 20 \log \left(\frac{10^4}{0.1} \right)$$

$$= 100 \text{ dB}$$

4) Calculate the output voltage of summing amplifier for the set of voltages. Use $R_f = 1\text{M}\Omega$ for all cases.

(a) $V_1 = +1\text{V}$, $V_2 = 2\text{V}$, $V_3 = 3\text{V}$, $R_1 = 500\text{K}$, $R_2 = 1\text{M}\Omega$
 $R_3 = 1\text{M}\Omega$


Soln

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

$$= - \left[\frac{1 \times 10^6}{500 \times 10^3} (1) + \frac{1 \times 10^6}{1 \times 10^6} (2) + \frac{1 \times 10^6}{1 \times 10^6} (3) \right]$$

$$= - [2 + 2 + 3]$$

$$= - 7\text{V.}$$

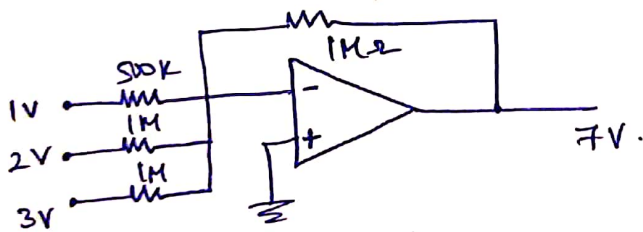

(b) $V_1 = -2\text{V}$, $V_2 = 3\text{V}$, $V_3 = 1\text{V}$, $R_1 = 200\text{K}$, $R_2 = 500\text{K}\Omega$, $R_3 = 1\text{M}\Omega$


Soln

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$


$$= - \left[\frac{1 \times 10^6}{200 \times 10^3} (-2) + \frac{1 \times 10^6}{500 \times 10^3} (3) + \frac{1 \times 10^6}{1 \times 10^6} (1) \right]$$

$$= - [-10 + 6 + 1]$$

$$= +3\text{V.}$$

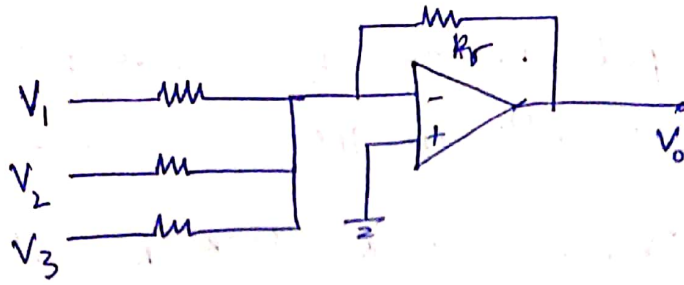

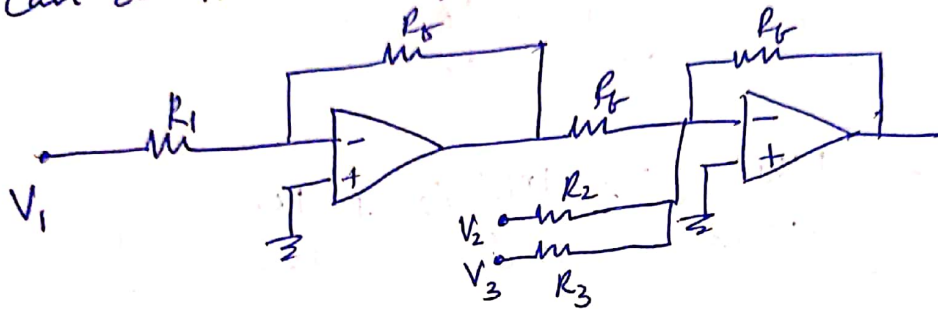⑧ The above circuit using 2-ideal op-amps can be written as,



5) Design a summer circuit using 2 ideal op-amp

$$V_0 = 2V_1 - 4V_2 + 6V_3$$


Soln Assume, $R_f = 10K\Omega$.

$$\frac{R_f}{R_1} = 2, \quad \frac{R_f}{R_2} = 4, \quad \frac{R_f}{R_3} = 6$$

$$R_1 = \frac{10 \times 10^3}{2} = 5K\Omega$$

$$R_2 = \frac{10 \times 10^3}{4} = 2.5K\Omega$$
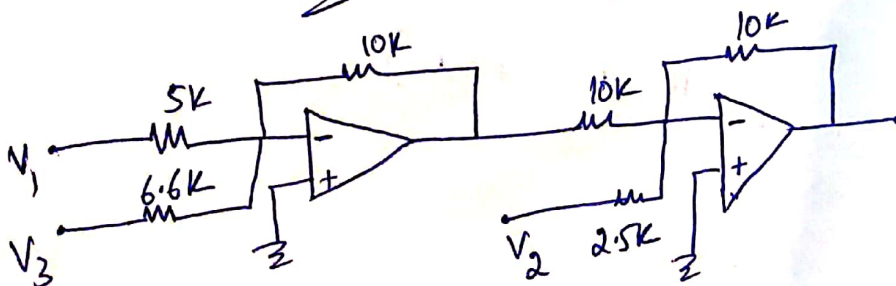
$$R_3 = \frac{10 \times 10^3}{6} = 6.6K\Omega$$



$$(b) \quad V_0 = V_1 + 3V_2 + 5V_3 - 7V_4 - 9V_5 - 11V_6$$

Assume $R_f = 10k\Omega$.

Soln.

$$\frac{R_f}{R_1} = 1 \Rightarrow R_1 = 10k\Omega$$


$$\frac{R_f}{R_2} = 3 \Rightarrow R_2 = \frac{10k\Omega}{3} = 3.3k\Omega$$

$$\frac{R_f}{R_3} = 5 \Rightarrow R_3 = 2k\Omega$$

$$\frac{R_f}{R_4} = 7 \Rightarrow R_4 = 1.57k\Omega$$

$$\frac{R_f}{R_5} = 9 \Rightarrow R_5 = 1.1k\Omega$$
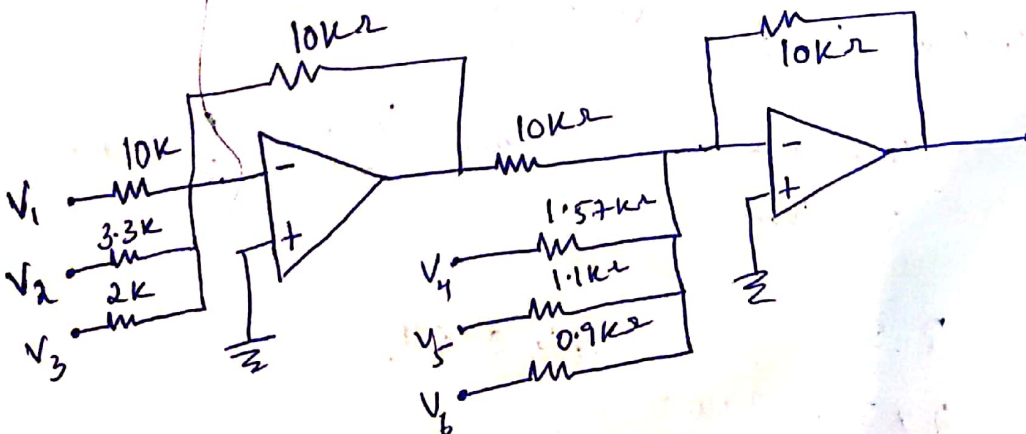
$$\frac{R_f}{R_6} = 11 \Rightarrow R_6 = 0.9k\Omega$$



- 6) An op-amp has a differential gain of 2×10^4 and a CMRR of 86 dB. Determine the output, if differential input is $10 \mu V$ and common mode ip is $10 mV$

Soln

$$V_o = A_d \cdot V_d + A_c \cdot V_c$$

$$CMRR = \frac{A_d}{A_c} \Rightarrow 20 \log\left(\frac{A_d}{A_c}\right) = 86$$

$$A_c = 1.0002$$

$$V_o = 2 \times 10^4 (10 \times 10^{-6}) + 1.0002 (10 \times 10^{-3})$$
$$= 0.21 V.$$


- 7) The output signal of an op-amp with a slew rate of $2.5 V/\mu s$ has a peak to peak value of $18 V$. Find the maximum frequency for undistorted output voltage.

Soln

$$f = \frac{\text{slew rate}}{2\pi V_m}, \quad V_m = \frac{V_{p-p}}{2} = \frac{18}{2} = 9 V$$

$$f = \frac{2.5}{2 \times 3.14 \times 9 \times 10^{-6}} = 44.2 \text{ KHz}$$

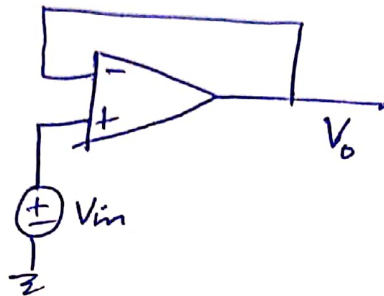- 8) In a voltage follower circuit, op-amp used is² ideal in all respect, except it has a finite gain A , Determine $\frac{V_o}{V_i}$. If $A = 1000$, calculate the error of the gain from that of the voltage follower with an ideal op-amp.



Soln

$$\frac{V_o}{V_i} = 1, \quad \therefore \text{it is a voltage follower.}$$

$$\% \text{ of error} = \left(1 - \frac{A}{A+1} \right) \times 100\%$$

$$= \left(1 - \frac{1000}{1001} \right)$$

$$= \underline{\underline{1}}$$

- 9) If slew rate of op-amp is $3\text{V}/\mu\text{s}$ and maximum output swing is $\pm 12\text{V}$, then calculate maximum frequency.

Soln

$$f_{\max} = \frac{3}{2 \times \pi \times 12 \times 10^{-6}} \quad (\mu\text{sec})$$

$$= \underline{\underline{39.8 \text{ kHz}}}$$